

Special Problem 3.1-10

Determine the voltages across, and currents through, **each** of the two **ideal diodes** in this circuit.

