

Special Problem 3.1-5

The diodes in this circuit are ideal.

Determine the current through, and voltage across, each diode.

