

Special Problem 3.1-6

The diodes in the circuit below are **ideal**.

Determine the **current through**, and **voltage across**, each of the two ideal diodes.

