

Special Problem 3.1-7

The diode in the circuit below is **ideal**.

Determine the **voltage** across and **current** through this diode.

