

Special Problem 3.1-9

In the circuit below, determine the **current through**, and **voltage across**, each of the two **ideal** diodes in the circuit below.

