

Special Problem 3.2-4

The **1K resistor** in the circuit below has **6 V** across it.

The junction diode has an **idealty** factor of $n = 1.0$.

What is the **scale current** I_s of this junction diode?

Hint: Do not use diode models (e.g., CVD) to analyze this circuit!

