

Special Problem 3.3-4

A junction diode has $I_s = 5 \times 10^{-9}$ and $n = 2$. For a small-signal application, find a piecewise-linear model (V_{D0} and r_d) which matches the behavior of the diode in a small region around a diode bias voltage of $V_D = 0.725$ V.