

Special Problem 3.5-3

The diodes in this bridge rectifier are **IDEAL**.

Note that the total source voltage consists of an AC and a DC (1.0 V) component.

- 1) Determine the transfer function of this rectifier circuit.
- 2) Carefully sketch below the output voltage $v_d(t)$ if the AC signal $v_s(t)$ is that shown below.
- 3) What is the **peak inverse voltage** if the input voltage shown below is applied (I want a **numerical** answer)?
- 4) Across which **diodes** does this peak inverse voltage appear?



