

Special Problem 3.5-5

The diode in the circuit below is **ideal**.

Determine the **transfer function** (i.e., the function that describes v_O in terms of v_I) for this circuit.

