

Special Problem 3.6-1

The diode in the circuit below has a Zener breakdown voltage of 18 volts.

Determine the transfer function $v_o = f(v_i)$ for the diode limiter shown below, and plot this transfer function.

