

Special Problem 3.6-6

The circuit below is a diode **limiter**.

Determine the **transfer function** (i.e., the function that describes V_o in terms of V_i) for this circuit.

Carefully plot this transfer function on the graph below. Label important values such as slopes, transition points, intercept points, etc.

