

Special Problem 3.6-7

The circuit below is a diode **limiter**.

The diode is **ideal**.

Determine the **transfer function** (i.e., the function that describes v_O in terms of v_I) for this circuit.

