

Special Problem 3.6-8

Below is a schematic for a limiter circuit.

Find an expression for v_o in terms of v_i .

