

**Special Problem 4.3-2**

Assume the MOSFET in the circuit below is in the **triode** region.

The current through the resistor  $R_1$  is **1 mA**.

- 1) Find the value of resistor  $R$ .
- 2) Determine if the assumption is correct.

**Hint:** Carefully consider numeric signs (+/-).

