

Special Problem 4.3-7

Assume Q_1 is in **Cutoff**, and Q_2 in **Triode** mode.

The **current** through the **2K resistor** is know to be **1.0 mA**.

- Determine the value of the **voltage** v_{G2} .
- Determine if **each** assumption is correct.

