

### Special Problem 4.6-2

For the circuit below,  $V_G$  is the DC bias at the gate,  $v_i$  is the small-signal input and  $v_o$  the small-signal output. The transistor is known to be in the **saturation** region.

The **capacitor** in the circuit is **extremely large**.

1) Draw the resulting **small-signal** circuit.

2) In terms of transconductance  $g_m$ , find the small-signal **gain**  $A_{v_o} = v_o/v_i$ .

**NOTE:** Do not attempt any **DC analysis**; provide your solutions directly in terms of  $g_m$ . Ignore the output resistance (i.e.,  $r_o = \infty$ ).

