

## Special Problem - 4.6-3

The capacitors in this circuit are very large.

Determine the small-signal voltage gain  $A_v = V_o/V_i$  of this amplifier.

Determine the small-signal input resistance of this amplifier.

