

Special Problem 4.6-4

The capacitor in the circuit below is **very large**.

Determine the **small-signal voltage gain** ($A_v = v_o/v_i$) of the **amplifier** below.

