

### Special Problem 5.4-5

Assume  $Q_1$  is in active and  $Q_2$  is in saturation.

A. Using these assumptions, determine the collector current and collector voltage for  $Q_1$ , and the drain current and drain voltage for  $Q_2$ .

B. Determine each if **each** assumption was correct.

