

Special Problem 10.3-3

Design and sketch a **CMOS** circuit that realizes the Boolean function

$$Y = (\overline{A + B}) + C.$$