

Special Problem 10.4-1

Design and sketch a **Pseudo-NMOS** circuit that realizes the Boolean function $Y = B + (\overline{AD + C})$.