

Special Problem 3.1 - 11

Determine the **current through**, and **voltage across**, the ideal diode in the circuit below.

