

**Special Problem 3.1-2**

The diodes in this circuit are ideal.

Determine the value of node voltages  $V_1$  and  $V_2$ , with respect to ground potential.

