

**Special Problem 3.1-3**

Determine the currents through, and voltages across, each of the two ideal diodes.

