

Special Problem 3.1-5

The diodes in this circuit are **ideal**.

Determine the **current through**, and **voltage across**, each diode.

