

Special Problem 3.1-8

Find the voltage across, and current through, each of the ideal diodes.

