

Special Problem 3.2 - 10

In the circuit below:

Junction diode D_1 has values $n = 1.000$ and $I_s = 5.11 \times 10^{-15}$ A.

Junction diode D_2 has values $n = 1.737$ and $I_s = 1.00 \times 10^{-8}$ A.

Using the **exact** junction diode equation (do **not** use diode models!), determine the value of **current I** and **voltage V** in the circuit below.

