

**Special Problem 3.2-4**

The **1K resistor** in the circuit below has **6 V** across it.

The junction diode has an **idealty** factor of  $n = 1.0$ .

What is the **scale current**  $I_s$  of this junction diode?

