

Special Problem 3.3 - 13

Using the **CVD model**, determine (approximately) the voltage across, and current through, the **junction diode** in the circuit below.

