

Special Problem 3.3 - 16

The current through a **junction diode** is known to be:

$$i_D(t) = 2.5 + 3.0 \cos \omega t \quad mA$$

This junction diode has an ideality factor of $n = 1.00$.

Determine (approximately) the **small-signal voltage** across the entire junction diode.