

### Special Problem 3.3-2

For the circuit given below, the voltage source is given as  $v_S = 7.4 + v_s(t)$ . The signal  $v_s(t)$  is a very small ( $|v_s(t)| < 10 \text{ mV}$ ) time-varying signal. When  $v_s(t) = 0$ , the output voltage is  $v_O = 1.4 \text{ V}$ . The output voltage can therefore be specified as  $v_O = 1.4 + v_o(t)$ , where  $v_o(t)$  is the small signal resulting from  $v_s(t)$ . Find  $v_o(t)$  in terms of  $v_s(t)$ . The ideality factor for the diodes is  $n=2$ .

