

Special Problem 3.4-11

The zener diode in the circuit below has a **breakdown voltage** of $V_{ZK} = 10.0 \text{ V}$.

Use the **zener CVD** model to approximately determine the **current through** (I_Z), and **voltage across** (V_Z), the zener diode in the circuit below.

