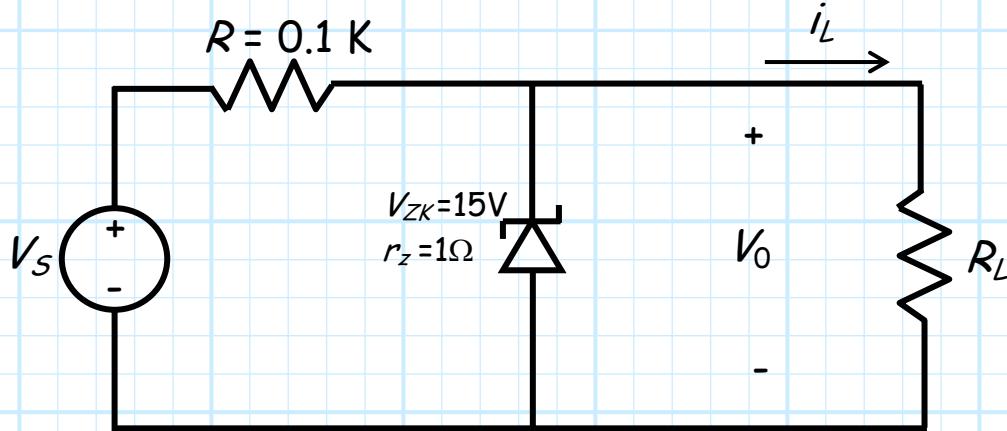


### Special Problem 3.4-12

Consider this shunt regulator, made with a zener diode whose breakdown voltage is 15.0 V, and whose incremental resistance is 1.0  $\Omega$  (i.e.,  $r_z = 0.001\text{K}$ ).



1. If the source voltage is 25.0 V (i.e.,  $V_S = 25.0\text{ V}$ ), determine the minimum value of load resistor  $R_L$  required for the output to be regulated at a voltage of  $V_0 = 15.0\text{ V}$ .
2. Determine the minimum value of source voltage  $V_S$  required to provide a regulated output voltage of  $V_0 = 15.0\text{ V}$  if the load current is  $i_L = 150\text{ mA}$ .
3. Determine the precise change in regulated output voltage  $V_0$  if the source voltage  $V_S$  is increased by 2.0 Volts.
4. Determine the precise change in the regulated output voltage  $V_0$  if the load current  $i_L$  is increased by 10 mA.

Hint: the answer to parts 3 and 4 is not zero.