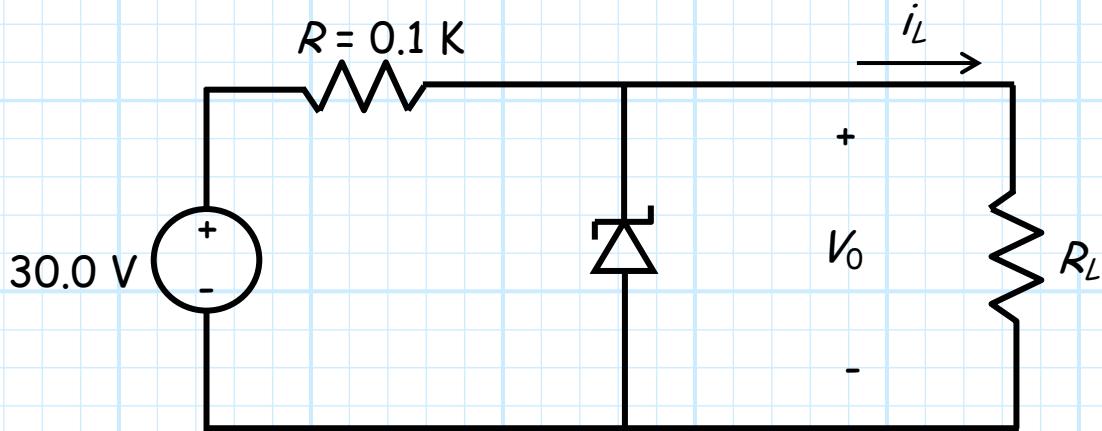


Special Problem 3.4-13

Consider this shunt regulator, where the zener diode and load resistor are yet to be determined.



Answer these four independent and uncoupled questions.

1. If the load resistor happens to have a value of $R_L = 0.4 \text{ K}$, determine the maximum value of zener diode breakdown voltage V_{ZK} such that the output to be regulated at a voltage of $V_0 = V_{ZK}$
2. If the zener diode happens to have a breakdown voltage of $V_{ZK} = 20.0 \text{ V}$ Determine the maximum value of load current i_L such that the output to be regulated at a voltage of $V_0 = 20.0 \text{ V}$
3. Say the load current i_L increases by 10 mA, resulting in a slight, 1.0 mV decrease of the regulated output voltage. Determine the dynamic (i.e., incremental) resistance of the zener diode.
4. Say the source voltage is increased from 30.0 V to 35.0 V, resulting in a slight, 10.0 mV increase of the regulated output voltage. Determine the line regulation of the regulator.