

Special Problem 3.4-4

The zener diode **breakdown voltage** is $V_{ZK} = 15.0 \text{ V}$.

Use the zener **CVD model** to determine the **voltage across** and **current through** the zener diode.

