

Special Problem 3.4-5

The Zener diode in the circuit below has a Zener breakdown voltage of $V_{ZK} = 10.0$ V.

Use the Zener CVD model to estimate the voltage across, and current through, the Zener diode (i.e., V_Z and I_Z).

