

### Special Problem 3.5-15

The diode in the circuit below is **IDEAL**.

The input to this circuit ( $v_I(t)$ ) is plotted below.

Determine the **Peak Inverse Voltage (PIV)** of the **ideal diode** in this circuit.

**Hint:** There is **no reason** to analyze the circuit for the **forward biased diode** case.

