

Special Problem 3.5-4

The diode in the circuit below is **ideal**.

Determine the **transfer function** of the circuit shown below.

In other words, determine V_o as a function of v_I .

