

Special Problem 3.5 -7

The diode in the circuit below is **ideal**.

Determine the **transfer function** $v_o = f(v_I)$ of this circuit.

