

Special Problem 3.6-9

The diode in the circuit below has a Zener breakdown voltage of **15.3 volts**.

Determine the **transfer function** $v_O = f(v_I)$ of the diode **limiter** shown below.

