

Special Problem 4.11-2

The MOSFET in the circuit below is a depletion type.

1) Determine the drain current.

2) Determine the source voltage.

