

**Special Problem 4.11-5**

Determine the drain voltage and the source voltage of the MOSFET.

