

Special Problem 4.3 -11

We know the current through R_3 is $i_3 = 2.0$ mA.

Assume Q_N is in **triode** mode.

Assume Q_P is in **saturation** mode.

A. Determine the value of resistor R_1 .

B. Determine each if **each** assumption was correct.

