

**Special Problem 4.3-3**

Assume that the MOSFET in the circuit below is in **triode** mode.

The current through resistor  $R_1$  is **1mA**.

Find the value of resistor  $R$ .

