

Special Problem 4.3-4

It is known that the current through resistor R_1 is $i_1 = 1 \text{ mA}$.

Assume that the MOSFET is in **triode** region.

- 1) Determine the value of resistor R_2 .
- 2) **Check** to see if the triode assumption was correct.

