

Special Problem 5.4-2

Assuming that Q_1 and Q_2 are both in the active mode, determine the **base currents** i_B and **collector voltages** V_C of each transistor.

Are the active assumptions correct? Provide **complete** numerical justification for your answer.

