

**Special Problem 5.4-4**

Assume  $Q_1$  is in cutoff and  $Q_2$  is in saturation.

1. Using these assumptions, determine the base, collector and emitter voltages for  $Q_1$ , and determine the base, collector and emitter currents for  $Q_2$ .

2. Determine if **each** assumption was correct.

