

**Special Problem 10.3-2**

Design and sketch a CMOS logic device that realizes the Boolean function:

1.  $\bar{Y} = B(A + C)$

2.  $Y = A + (\overline{BC})\bar{D} + \bar{E}$