

Special Problem 3.1-1

For the circuit given below, assume the diodes are **ideal**. Find the currents through, and voltages across, each of the two diodes.

