

Special Problem 3.1-3

Determine the currents through, and voltages across, each of the two **ideal** diodes.

